

# Phase Shifter

A dedicated phaser module for the FORMANT is the icing on the cake, musically enhancing smaller FORMANT versions (e.g., the “Mini-FORMANT”) in particular.

While the FORMANT VCO offers a distinctive feature compared to many commercial units—namely, pulse width modulation (PWM) for the square wave, which allows a phasing effect to be created using just a single VCO—this effect does not apply to the other waveforms. It is precisely in this context that a dedicated phase shifter module has proven advantageous.

Unlike high-pass and low-pass filters, all-pass filters maintain a constant output signal amplitude across a wide frequency range. Instead, they introduce a frequency-dependent phase shift between the input and output signals. This effect can be utilized to delay analog signals; consequently, such phase shifters are frequently employed in music electronics to produce the characteristic phasing effect.

Figure 1 illustrates how easily an all-pass filter can be implemented. In this circuit, the phase shift between the input and output signals depends solely on the values of resistor R and capacitor C. The diagram shows the phase shift as a function of frequency. It is evident from this that the circuit is a first-order all-pass filter, as the phase shift ranges from  $0^\circ$  to  $180^\circ$ .

Figure 2 shows the phaser circuit. IC1a ensures high input impedance. Its output drives a six-stage phase-shift chain constructed using operational amplifiers IC1b through IC2c. Field-effect transistors T1 through T6 operate as voltage-controlled resistors. The higher the drain-source resistance, the smaller the phase shift. Operational amplifier IC2d sums the phase-shifted and non-phase-shifted input signals, while potentiometer P2 allows the mini-phaser's output amplitude to be matched to various amplifier sensitivities. To produce a phasing effect, a triangle-wave generator is also required to drive the gates of FETs T1 through T6; this is built using operational amplifiers IC3 and IC4. The first operational amplifier functions as a non-inverting Schmitt trigger, with its hysteresis determined primarily by the positive feedback provided by resistors R26 and R27. It receives its input signal from an integrator consisting of the frequency-determining components R28, P1, C9, and IC4. The amplitude of the triangle-wave voltage at the integrator output ranges from -6 V to -4 V, as the FET gates must be negatively biased relative to the source. The triangle-wave generator can be disabled, allowing for manual phasing via potentiometer P3; this is particularly recommended for drums, as it enables the phasing effect to be optimally matched to the drummer's tempo. Potentiometer P4 controls the phasing depth—that is, the balance between the phase-shifted signal and the original signal. The phasing effect is most pronounced when the triangle-wave generator oscillates at a frequency of approximately 0.5 Hz to 1 Hz. If the frequency of this generator is increased to approximately 4 Hz, the phasing effect is lost, but a new one emerges: phase vibrato.

To compensate for the tolerances of the field-effect transistors, potentiometer P5 is provided.

# The Front Panel

Figure 4 shows the front panel design for the phase shifter.

A single-pole miniature toggle switch suffices for the "automatic/manual frequency modulation" function (S2). The mounting holes for the potentiometers are designed for types with 6 mm shafts (P1 = automatic frequency modulation, P3 = manual frequency modulation, P4 = rate).

Switch S1 (on/off) allows the phasing effect to be switched off without having to unplug patch cords. Alternatively, this switch can be used to preset the desired phasing depth.

# The Circuit Board

The circuit board layout (Figure 6) has been redesigned specifically for use in 19" rack-mount enclosures and card magazines. The additional wiring for the power supply lines is shown in Figure 5. A 31-pin connector strip is used. Otherwise, the component placement diagram is identical to that shown in Figure 3. 4

# BOM

## Resistors:

R1, R2 = 100k

R3, R4, R5, R6, R7, R8, R9, R10, R11, R12, R13, R14, R21, R22 = 22k

R15, R16, R17, R18, R19, R20, R23, R35 = 10k

R24, R25 = 33k

R26 = 330k

R27 = 1M

R28, R36 = 4k7

R29 = 10M

R30 = 12k

R31 = 3k9

R32, R34 = 47k

R33 = 470k

P1 = 470 K lin.

P2,P5 = 50K trimmer

P3 = 10k lin.

P4 = 10k log.

## Capacitors:

C1 = 470n  
C2 = 4 $\mu$ 7/30 V tantalum  
C3 = 1n  
C4 = 470n  
C5 = 330n  
C6 = 150n  
C7 = 100n  
C8 = 47n  
C9 = 4 $\mu$ 7/16V tantalum

## Semiconductor:

IC1, IC2 = 324 (better XR 4212)  
IC3, IC4 = 741  
T1, T2, T3, T4, T5, T6 = BF 245C

## Miscellaneous:



S1, S2 = Switch 1 x Um


## Figures


- Figure 1. Basic circuit configuration of a high-pass filter. The diagram shows the phase shift as a function of frequency.
- Figure 2. Complete phaser circuit.
- Figure 3. PCB layout and component placement diagram for the circuit shown in Figure 2.
- Figure 4. Proposed front panel design for the phase shifter.
- Figure 5. The supply voltage for the phaser is +12 V. The required voltage can be derived from the +15 V FORMANT supply voltage using just a few components.
- Figure 6. PCB layout and component placement diagram for the circuit shown in Figure 2. The PCB is in Eurocard format and includes the additional circuitry from Figure 5.


1

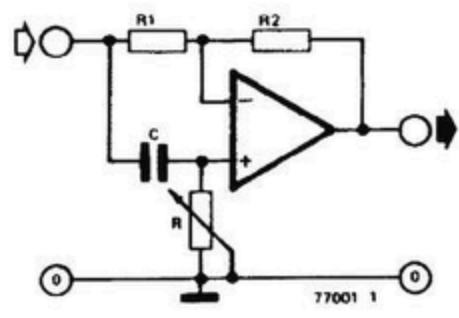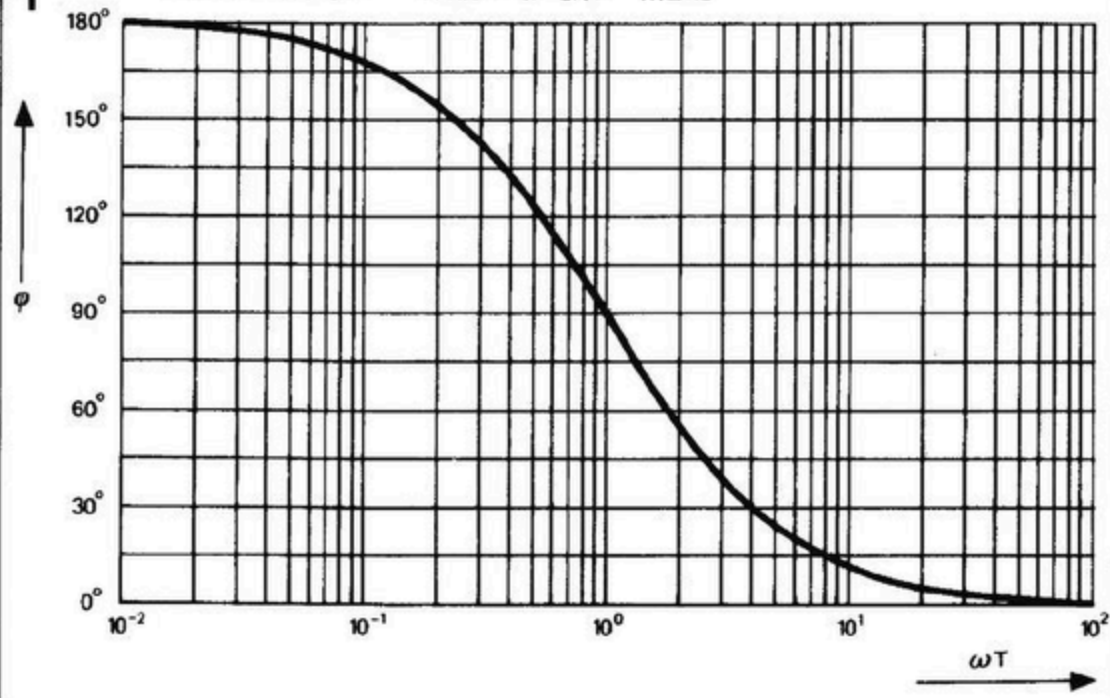$\varphi = 180^\circ - 2 \arctan \omega T$      $T = R.C$  ;     $\omega = 2\pi f$      $R1 = R2$



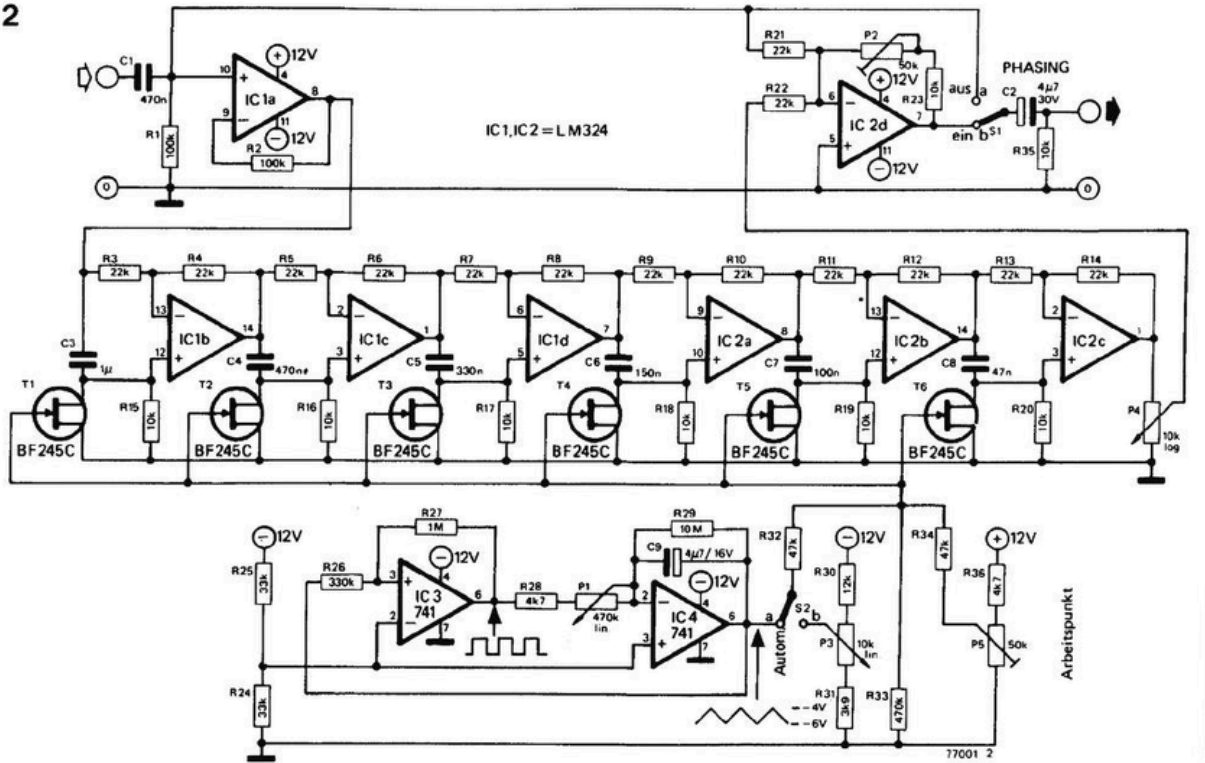

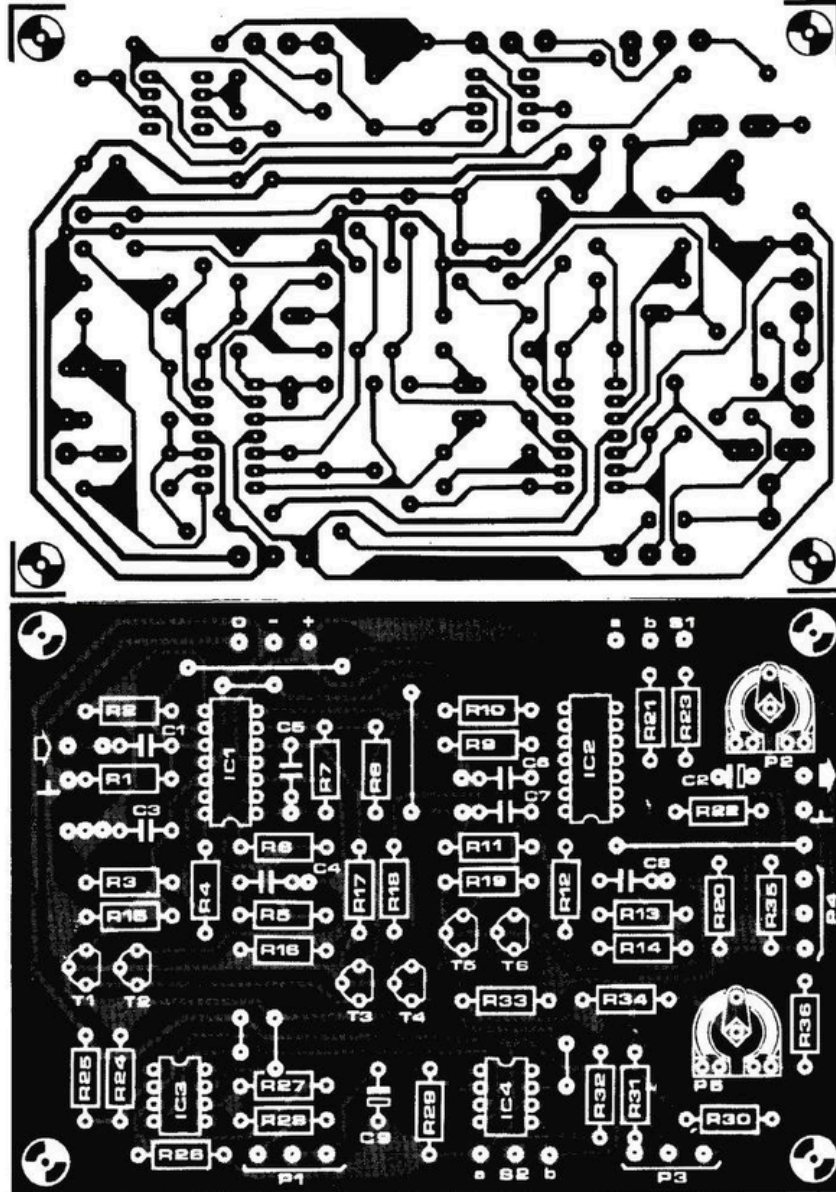

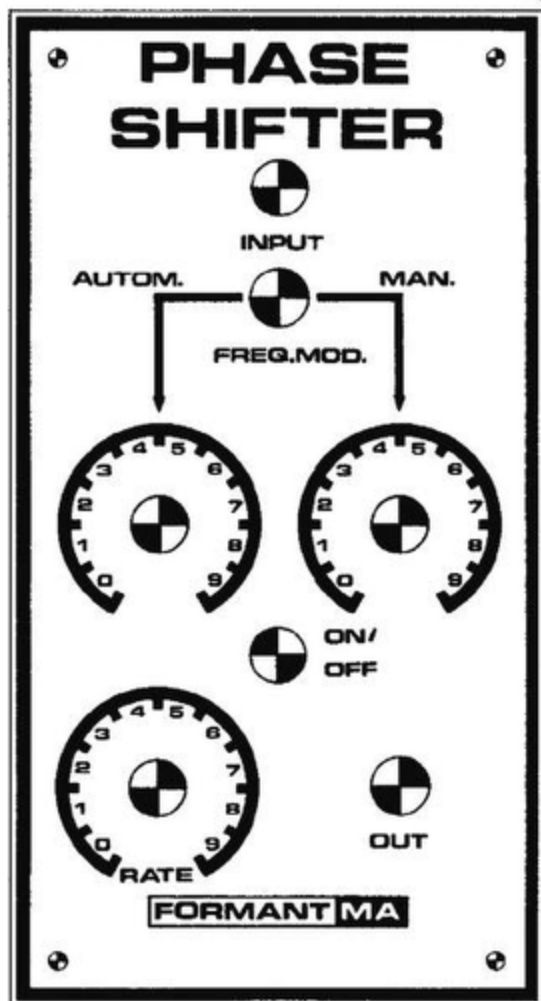

5

